

# Circuits and Transforms

## EE3900: Linear Systems and Signal Processing

### Indian Institute of Technology Hyderabad

Donal Loitam  
AI21BTECH11009

#### 1. DEFINITIONS

1.1 The unit step function is defined as

$$u(t) = \begin{cases} 1 & t > 0 \\ \frac{1}{2} & t = 0 \\ 0 & t < 0 \end{cases} \quad (1.1)$$

1.2 The Laplace transform of  $g(t)$  is defined as

$$G(s) = \int_{-\infty}^{\infty} g(t)e^{-st} dt \quad (1.2)$$

#### 2. LAPLACE TRANSFORM

2.1. In the circuit, the switch S is connected to position P for a long time so that the charge on the capacitor becomes  $q_1 \mu\text{C}$ . Then S is switched to position Q. After a long time, the charge on the capacitor is  $q_2 \mu\text{C}$

2.2. Draw the circuit using latex-tikz

**Solution:**


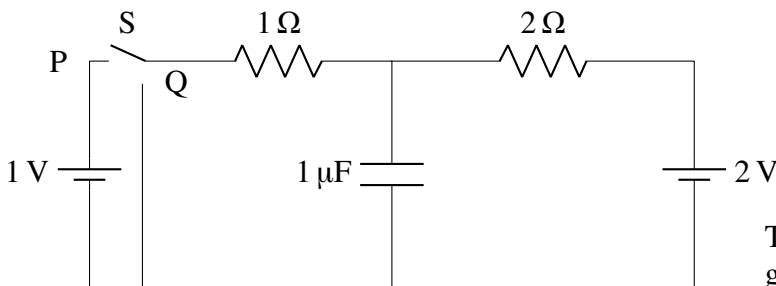


Fig. 2.2. Circuit diagram of the circuit in question

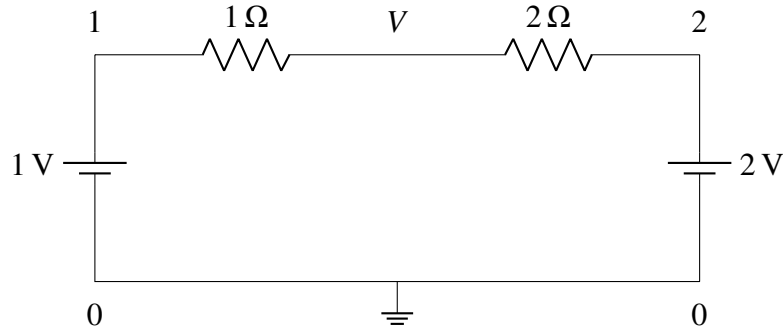2.3. Find  $q_1$

**Solution:** After a long time, when steady state is achieved, a capacitor behaves like an open circuit, i.e., current passing through it is zero



By Kirchoff's junction law, we get

$$\frac{V-1}{1} + \frac{V-2}{2} = 0 \quad (2.1)$$

$$\Rightarrow V = \frac{4}{3} \text{ V} \quad (2.2)$$

$$\Rightarrow q_1 = CV = \frac{4}{3} \mu\text{C} \quad (2.3)$$

2.4. Show that the Laplace transform of  $u(t)$  is  $\frac{1}{s}$  and find the ROC

**Solution:** The Laplace transform of  $u(t)$  is given by

$$\mathcal{L}\{u(t)\} = \int_{-\infty}^{\infty} u(t)e^{-st} dt \quad (2.4)$$

$$= \int_0^{\infty} e^{-st} dt \quad (2.5)$$

$$= \lim_{R \rightarrow \infty} \frac{1 - e^{-sR}}{s} \quad (2.6)$$

This limit is finite only if  $\Re(s) > 0$ , which is going to be its ROC

Therefore

$$u(t) \xleftrightarrow{\mathcal{L}} \frac{1}{s} \quad \Re(s) > 0 \quad (2.7)$$

2.5. Show that

$$e^{-at}u(t) \xleftrightarrow{\mathcal{L}} \frac{1}{s+a} \quad a > 0 \quad (2.8)$$

and find the ROC

**Solution:** The Laplace transform of  $e^{-at}u(t)$  for  $a > 0$  is given by

$$\mathcal{L}\{u(t)\} = \int_{-\infty}^{\infty} e^{-at}u(t)e^{-st}dt \quad (2.9)$$

$$= \int_0^{\infty} e^{-(s+a)t}dt \quad (2.10)$$

$$= \lim_{R \rightarrow \infty} \frac{1 - e^{-(s+a)R}}{s + a} \quad (2.11)$$


This limit is finite only if  $\Re(s + a) > 0$ , which is going to be its ROC

Therefore

$$e^{-at}u(t) \xleftrightarrow{\mathcal{L}} \frac{1}{s + a} \quad \Re(s) > -a \quad (2.12)$$

since  $a$  is real

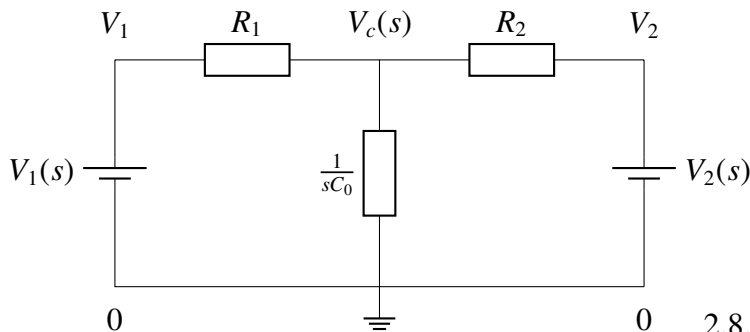2.6. Now consider the following resistive circuit transformed from Fig. 2.2



where

$$u(t) \xleftrightarrow{\mathcal{L}} V_1(s) \quad (2.13)$$

$$2u(t) \xleftrightarrow{\mathcal{L}} V_2(s) \quad (2.14)$$

Find the voltage across the capacitor  $V_C(s)$

**Solution:**

$$V_1(s) = \frac{1}{s} \quad \Re(s) > 0 \quad (2.15)$$

$$V_2(s) = \frac{2}{s} \quad \Re(s) > 0 \quad (2.16)$$

By Kirchoff's junction law, we get

$$\frac{V_c - V_1}{R_1} + \frac{V_c - V_2}{R_2} + \frac{V_c - 0}{\frac{1}{sC_0}} = 0 \quad (2.17)$$

$$\Rightarrow V_c \left( \frac{1}{R_1} + \frac{1}{R_2} + sC_0 \right) = \frac{V_1}{R_1} + \frac{V_2}{R_2} \quad (2.18)$$

$$\Rightarrow V_c(s) = \frac{\frac{1}{sR_1} + \frac{2}{sR_2}}{\frac{1}{R_1} + \frac{1}{R_2} + sC_0} \quad (2.19)$$

$$= \frac{\frac{1}{R_1C_0} + \frac{2}{R_2C_0}}{s \left( s + \frac{1}{R_1C_0} + \frac{1}{R_2C_0} \right)} \quad (2.20)$$

2.7. Find  $v_c(t)$

**Solution:**

$$V_c(s) = \frac{\frac{1}{R_1C_0} + \frac{2}{R_2C_0}}{\frac{1}{R_1C_0} + \frac{1}{R_2C_0}} \left( \frac{1}{s} - \frac{1}{s + \frac{1}{R_1C_0} + \frac{1}{R_2C_0}} \right) \quad (2.21)$$

$$= \frac{\frac{1}{R_1} + \frac{2}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2}} \left( \frac{1}{s} - \frac{1}{\frac{1}{C_0} \left( \frac{1}{R_1} + \frac{1}{R_2} \right) + s} \right) \quad (2.22)$$

Taking the inverse Laplace transform in (2.22),

$$V(s) \xleftrightarrow{\mathcal{L}} \frac{2R_1 + R_2}{R_1 + R_2} u(t) \left( 1 - e^{-\left( \frac{1}{R_1} + \frac{1}{R_2} \right) \frac{t}{C_0}} \right) \quad (2.23)$$

$$= \frac{4}{3} \left( 1 - e^{-(1.5 \times 10^6)t} \right) u(t) \quad (2.24)$$

The python code codes/2.6.py plots the graph below.

2.8. Verify your result using ngspice

### 3. INITIAL CONDITIONS

3.1. Find  $q_2$  in Fig. 2.2

**Solution:** After a long time, when steady state is achieved, a capacitor behaves like an open circuit, i.e., current passing through it is zero. By Kirchoff's junction law, we get

$$\frac{V - 0}{1} + \frac{V - 2}{2} = 0 \quad (3.1)$$

$$\Rightarrow V = \frac{2}{3} V \quad (3.2)$$

$$\Rightarrow q_2 = CV = \frac{2}{3} \mu C \quad (3.3)$$

3.2. Draw the equivalent  $s$ -domain resistive circuit when S is switched to position Q. Use variables


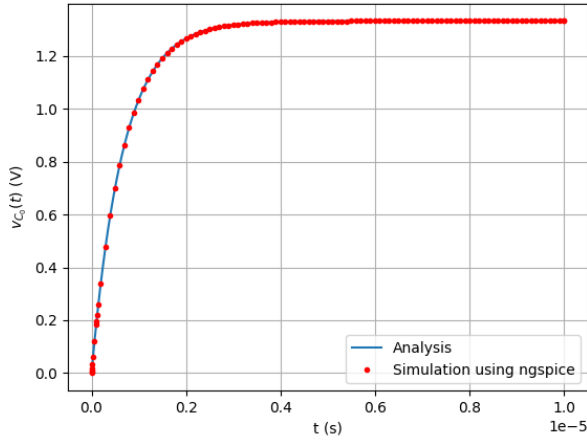


Fig. 2.7.  $v_{C_0}(t)$  before the switch is flipped

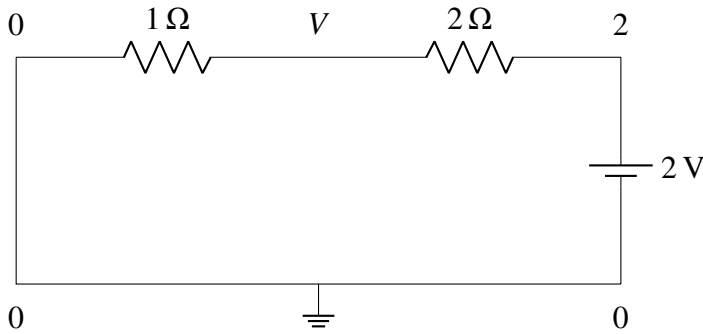

$R_1, R_2, C_0$  for the passive elements. Use latex-tikz

**Solution:**

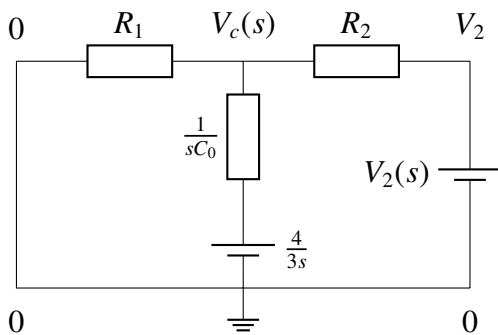


Fig. 3.2. Circuit diagram in  $s$ -domain

The battery  $\frac{4}{3s}$  corresponds to the initial potential difference of  $\frac{4}{3}$  V across the capacitor just before switching it to Q

3.3. Find  $V_c(s)$

**Solution:** By Kirchoff's junction law, we get

$$\frac{V_c - 0}{R_1} + \frac{V_c - V_2}{R_2} + \frac{V_c - \frac{4}{3s}}{\frac{1}{sC_0}} = 0 \quad (3.4)$$

$$\Rightarrow V_c \left( \frac{1}{R_1} + \frac{1}{R_2} + sC_0 \right) = \frac{V_2}{R_2} + \frac{4}{3}C_0 \quad (3.5)$$

$$\Rightarrow V_c(s) = \frac{\frac{2}{sR_2} + \frac{4}{3}C_0}{\frac{1}{R_1} + \frac{1}{R_2} + sC_0} \quad (3.6)$$

$$= \frac{\frac{2}{R_2C_0} + \frac{4}{3}s}{s \left( s + \frac{1}{R_1C_0} + \frac{1}{R_2C_0} \right)} \quad (3.7)$$

3.4. Find  $v_c(t)$ . Plot using Python

**Solution:** On performing partial fraction decomposition

$$V_c(s) = \frac{4}{3} \left( \frac{1}{s + \frac{1}{R_1C_0} + \frac{1}{R_2C_0}} \right) + \frac{\frac{2}{R_2C_0}}{\frac{1}{R_1C_0} + \frac{1}{R_2C_0}} \left( \frac{1}{s} - \frac{1}{s + \frac{1}{R_1C_0} + \frac{1}{R_2C_0}} \right) \quad (3.8)$$

for  $\Re(s) > 0$

On taking the inverse Laplace transform, we get

$$v_c(t) = \frac{4}{3} e^{-\left(\frac{1}{R_1} + \frac{1}{R_2}\right)\frac{t}{C_0}} u(t) + \frac{2R_1}{R_1 + R_2} \left( u(t) - e^{-\left(\frac{1}{R_1} + \frac{1}{R_2}\right)\frac{t}{C_0}} u(t) \right) \quad (3.9)$$

Substitute the values  $R_1 = 1 \Omega, R_2 = 2 \Omega, C_0 = 1 \mu\text{F}$

$$v_c(t) = \frac{4}{3} e^{-\frac{3}{2} \times 10^6 t} u(t) + \frac{2}{3} \left( 1 - e^{-\frac{3}{2} \times 10^6 t} \right) u(t) \quad (3.10)$$

$$= \frac{2}{3} \left( 1 + e^{-\frac{3}{2} \times 10^6 t} \right) u(t) \text{ V} \quad (3.11)$$

The Python code codes/3.4.py plots the graph below.

3.5. Verify your result using ngspice **Solution:** The ngspice script codes/3.5.cir simulates the given circuit and the generated output is depicted in Fig. (3.4).

3.6. Find  $v_c(0^-)$ ,  $v_c(0^+)$  and  $v_c(\infty)$

**Solution:** At  $t = 0^-$ , the switch still hasn't been switched to Q and the circuit is in steady state

$$v_c(0^-) = \frac{4}{3} \text{ V} \quad (3.12)$$

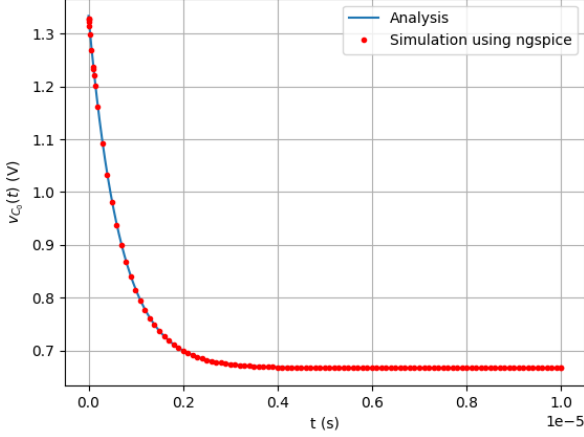


Fig. 3.4.  $v_{C_0}(t)$  after the switch is flipped

For  $t \geq 0$ , we can use the above formula

$$v_c(0^+) = \lim_{t \rightarrow 0^+} v_c(t) = \frac{4}{3} \text{ V} \quad (3.13)$$

$$v_c(\infty) = \lim_{t \rightarrow \infty} v_c(t) = \frac{2}{3} \text{ V} \quad (3.14)$$

3.7. Obtain Fig. 3.2 using the equivalent differential equation

**Solution:** Using Kirchoff's junction law

$$\frac{v_c(t) - 0}{R_1} + \frac{v_c(t) - v_2(t)}{R_2} + \frac{dq}{dt} = 0 \quad (3.15)$$

where  $q(t)$  is the charge on the capacitor

On taking the Laplace transform on both sides of this equation

$$\frac{V_c(s) - 0}{R_1} + \frac{V_c(s) - V_2(s)}{R_2} + (sQ(s) - q(0^-)) = 0 \quad (3.16)$$

But  $q(0^-) = \frac{4}{3}C_0$  and

$$q(t) = C_0 v_c(t) \quad (3.17)$$

$$\Rightarrow Q(s) = C_0 V_c(s) \quad (3.18)$$

Thus

$$\frac{V_c(s) - 0}{R_1} + \frac{V_c(s) - V_2(s)}{R_2} + \quad (3.19)$$

$$\left( sC_0 V_c(s) - \frac{4}{3}C_0 \right) = 0 \quad (3.20)$$

$$\Rightarrow \frac{V_c(s) - 0}{R_1} + \frac{V_c(s) - V_2(s)}{R_2} + \frac{V_c(s) - \frac{4}{3s}}{\frac{1}{sC_0}} = 0 \quad (3.21)$$

which is the same equation as the one we obtained from Fig. 3.2

The equivalent circuit in the  $t$ -domain is shown below.

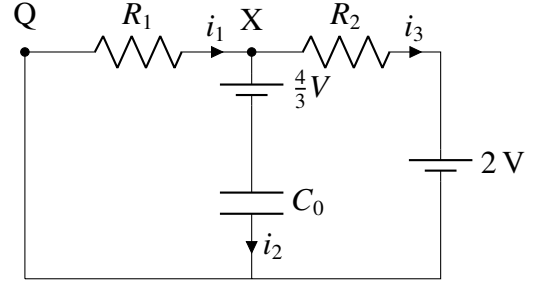


Fig. 3.7.

#### 4. BILINEAR TRANSFORM

4.1. In Fig. 2.2, consider the case when  $S$  is switched to  $Q$  right in the beginning. Formulate the differential equation

**Solution:** The differential equation is the same as before

$$\frac{v_c(t) - 0}{R_1} + \frac{v_c(t) - v_2(t)}{R_2} + \frac{dq}{dt} = 0 \quad (4.1)$$

$$\text{i.e., } \frac{v_c(t)}{R_1} + \frac{v_c(t) - v_2(t)}{R_2} + C_0 \frac{dv_c}{dt} = 0 \quad (4.2)$$

but with a different initial condition

$$q(0^-) = q(0) = 0 \quad (4.3)$$

4.2. Find  $H(s)$  considering the output voltage at the capacitor

**Solution:** The transfer function of a control system is defined as the ratio of the Laplace transform of the output variable to Laplace transform of the input variable assuming all initial conditions to be zero.

On taking the Laplace transform on both sides of this equation

$$\frac{V_c(s)}{R_1} + \frac{V_c(s) - V_2(s)}{R_2} + sQ(s) - 0 = 0 \quad (4.4)$$

$$\Rightarrow V_c(s) \left( \frac{1}{R_1} + \frac{1}{R_2} \right) + sC_0 V_c(s) = \frac{V_2(s)}{R_2} \quad (4.5)$$

$$\Rightarrow \frac{V_c(s)}{V_2(s)} = \frac{\frac{1}{R_2}}{\frac{1}{R_1} + \frac{1}{R_2} + sC_0} \quad (4.6)$$

The transfer function is thus

$$H(s) = \frac{\frac{1}{R_2 C_0}}{s + \frac{1}{R_1 C_0} + \frac{1}{R_2 C_0}} \quad (4.7)$$

On substituting the values, we get

$$H(s) = \frac{5 \times 10^5}{s + 1.5 \times 10^6} \quad (4.8)$$

4.3. Plot  $H(s)$ . What kind of filter is it?

**Solution:** Download the following Python code that plots Fig. 4.3

```
wget https://github.com/Donal-08/EE3900/
raw/main/Circuit/codes/4.3.py
```

Run the codes by executing

```
python 4.3.py
```

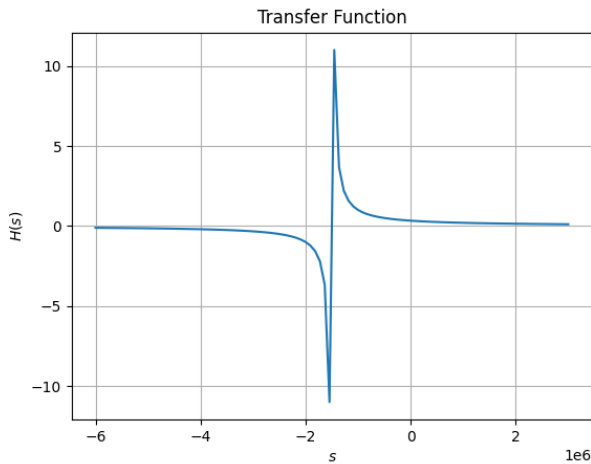


Fig. 4.3. Plot of  $H(s)$

Consider the frequency-domain transfer function by putting  $s = j\omega$

$$H(j\omega) = \frac{5 \times 10^5}{j\omega + 1.5 \times 10^6} \quad (4.9)$$

$$\Rightarrow |H(j\omega)| = \frac{5 \times 10^5}{\sqrt{\omega^2 + 2.25 \times 10^{12}}} \quad (4.10)$$

As  $\omega$  increases,  $|H(j\omega)|$  decreases

In other words, the amplitude of high-frequency signals gets diminished and they get filtered out

Therefore, this is a low-pass filter

4.4. Using trapezoidal rule for integration, formulate the difference equation by considering

$$y(n) = y(t)|_{t=n} \quad (4.11)$$

**Solution:**

$$\frac{v_c(t)}{R_1} + \frac{v_c(t) - v_2(t)}{R_2} + C_0 \frac{dv_c}{dt} = 0 \quad (4.12)$$

$$\Rightarrow C_0 \frac{dv_c}{dt} = \frac{2u(t) - v_c(t)}{R_2} - \frac{v_c(t)}{R_1} \quad (4.13)$$

$$\Rightarrow v_c(t)|_{t=n}^{n+1} = \int_n^{n+1} \left( \frac{2u(t) - v_c(t)}{R_2 C_0} - \frac{v_c(t)}{R_1 C_0} \right) dt \quad (4.14)$$

By the trapezoidal rule of integration

$$\int_a^b f(t) dt \approx \frac{b-a}{2} (f(a) + f(b)) \quad (4.15)$$

Consider  $y(t) = v_c(t)$

$$y(n+1) - y(n) = \frac{1}{R_2 C_0} (u(n) + u(n+1)) - \frac{1}{2} (y(n+1) + y(n)) \left( \frac{1}{R_1 C_0} + \frac{1}{R_2 C_0} \right) \quad (4.16)$$

Thus, the difference equation is

$$\begin{aligned} y(n+1) & \left( 1 + \frac{1}{2R_1 C_0} + \frac{1}{2R_2 C_0} \right) \\ &= y(n) \left( 1 - \frac{1}{2R_1 C_0} - \frac{1}{2R_2 C_0} \right) \\ &+ \frac{1}{R_2 C_0} (u(n) + u(n+1)) \end{aligned} \quad (4.17)$$

4.5. Find  $H(z)$

**Solution:** Let  $\mathcal{Z}\{y(n)\} = Y(z)$

On taking the Z-transform on both sides of the difference equation

$$\begin{aligned} zY(z) & \left( 1 + \frac{1}{2R_1 C_0} + \frac{1}{2R_2 C_0} \right) \\ &= Y(z) \left( 1 - \frac{1}{2R_1 C_0} - \frac{1}{2R_2 C_0} \right) \\ &+ \frac{1}{R_2 C_0} \left( \frac{1}{1-z^{-1}} + \frac{z}{1-z^{-1}} \right) \end{aligned} \quad (4.18)$$

$$\begin{aligned} Y(z) & \left( z + \frac{z}{2R_1 C_0} + \frac{z}{2R_2 C_0} - 1 + \frac{1}{2R_1 C_0} + \frac{1}{2R_2 C_0} \right) \\ &= \frac{1}{R_2 C_0} \frac{1+z}{1-z^{-1}} \end{aligned} \quad (4.19)$$

Also

$$v_2(t) = 2 \quad \forall t \geq 0 \quad (4.20)$$

$$\Rightarrow x(n) = 2u(n) \quad (4.21)$$

$$\Rightarrow X(z) = \frac{2}{1-z^{-1}} \quad |z| > 1 \quad (4.22)$$

Thus, the transfer function in  $z$ -domain is

$$H(z) = \frac{Y(z)}{X(z)} \quad (4.23)$$

$$= \frac{\frac{1+z}{2R_2C_0}}{z + \frac{z}{2R_1C_0} + \frac{z}{2R_2C_0} - 1 + \frac{1}{2R_1C_0} + \frac{1}{2R_2C_0}} \quad (4.24)$$

$$= \frac{\frac{1+z^{-1}}{2R_2C_0}}{1 + \frac{1}{2R_1C_0} + \frac{1}{2R_2C_0} - z^{-1} + \frac{z^{-1}}{2R_1C_0} + \frac{z^{-1}}{2R_2C_0}} \quad (4.25)$$

On substituting the values

$$H(z) = \frac{2.5 \times 10^5(1 + z^{-1})}{7.5 \times 10^5 + 1 + (7.5 \times 10^5 - 1)z^{-1}} \quad (4.26)$$

with the ROC being

$$|z| > \max\left(1, \left|\frac{7.5 \times 10^5 - 1}{7.5 \times 10^5 + 1}\right|\right) \quad (4.27)$$

$$\Rightarrow |z| > 1 \quad (4.28)$$

4.6. How can you obtain  $H(z)$  from  $H(s)$ ?

**Solution:** The Z-transform can be obtained from the Laplace transform by the substitution

$$s = \frac{2}{T} \frac{1 - z^{-1}}{1 + z^{-1}} \quad (4.29)$$

where  $T$  is the step size of the trapezoidal rule (1 in our case)

This is known as the bilinear transform

Thus

$$H(z) = \frac{\frac{1}{R_2C_0}}{2 \frac{1-z^{-1}}{1+z^{-1}} + \frac{1}{R_1C_0} + \frac{1}{R_2C_0}} \quad (4.30)$$

$$= \frac{\frac{1+z^{-1}}{2R_2C_0}}{1 - z^{-1} + \left(\frac{1}{2R_1C_0} + \frac{1}{2R_2C_0}\right)(1 + z^{-1})} \quad (4.31)$$

$$= \frac{\frac{1+z^{-1}}{2R_2C_0}}{1 + \frac{1}{2R_1C_0} + \frac{1}{2R_2C_0} - z^{-1} + \frac{z^{-1}}{2R_1C_0} + \frac{z^{-1}}{2R_2C_0}} \quad (4.32)$$

$$= \frac{2.5 \times 10^5(1 + z^{-1})}{7.5 \times 10^5 + 1 + (7.5 \times 10^5 - 1)z^{-1}} \quad (4.33)$$

which is the same as what we obtained earlier